



INDRAPRASTHA INSTITUTE *of*  
INFORMATION TECHNOLOGY  
DELHI

Department  
of  
Electronics & Communication Engineering

ECE111|Digital Circuits

**Dr. G.S. Visweswaran**

Lab\_1:

Student Name : Aayush Gakhar  
Roll No. : 2020006  
Date : 21/1/2021


Aim: Creating a simple circuit using breadboard

Components/ICs Used: Breadboard, Red LED, 1 kΩ Resistor, [5.5 Power Supply], Wire, slideswitch

Link of TINKERCAD Workspace: <https://www.tinkercad.com/things/1eF7JFtlWN8>

Pin Diagram of the IC (If Applicable)

Circuit Diagram: Screen shot

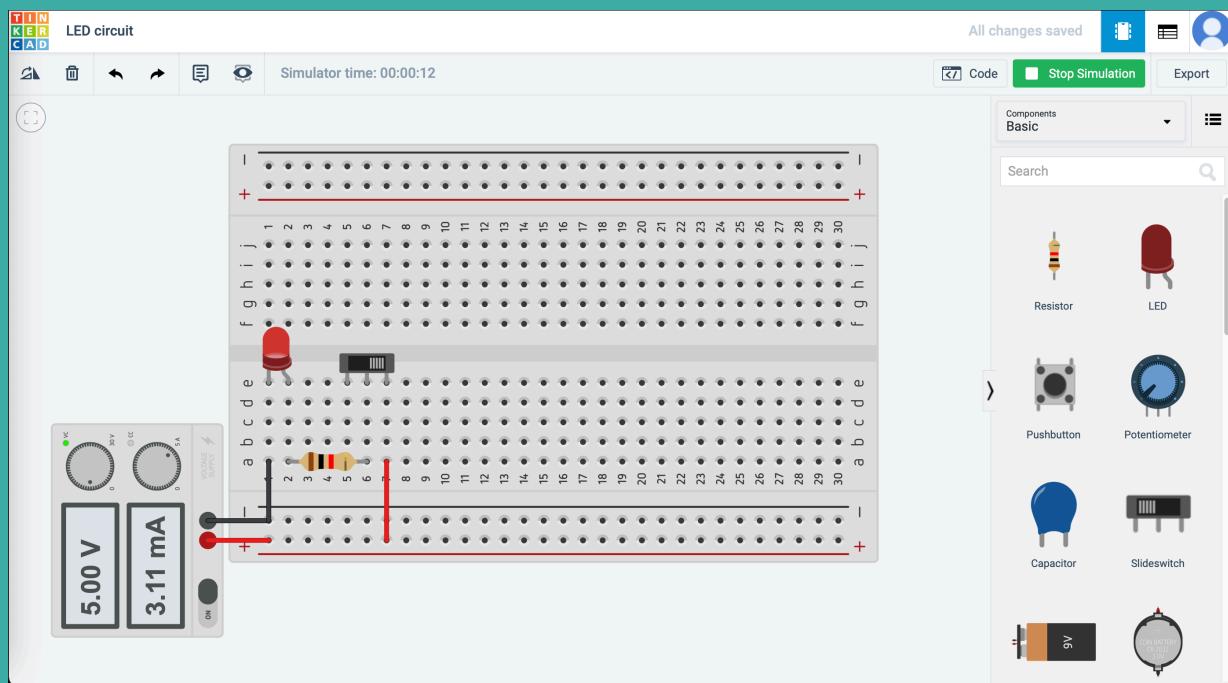

Truth Table:

Switch	LED
0	0
1	1

K maps (If Applicable):


Observations/Results: We can conclude that the LED glows when switch is on and vice versa.

Aim: Testing output of AND gate using Tinkercad


Components/ICs Used: Breadboard, Red LED, 1 kΩ Resistor, [5,5 Power Supply], Wire, slideswitch, Quad AND gate(74HC08)

Link of TINKERCAD Workspace: <https://www.tinkercad.com/things/1oYHVhukjBu>

Pin Diagram of the IC (If Applicable):

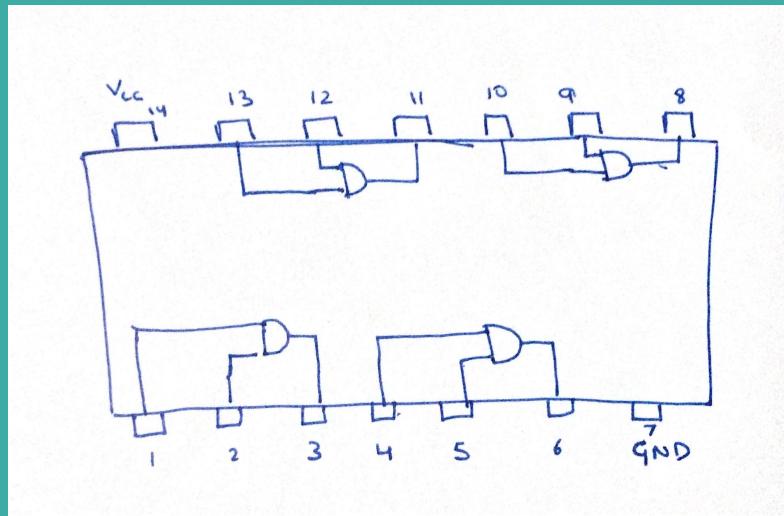

Circuit Diagram: Screen shot

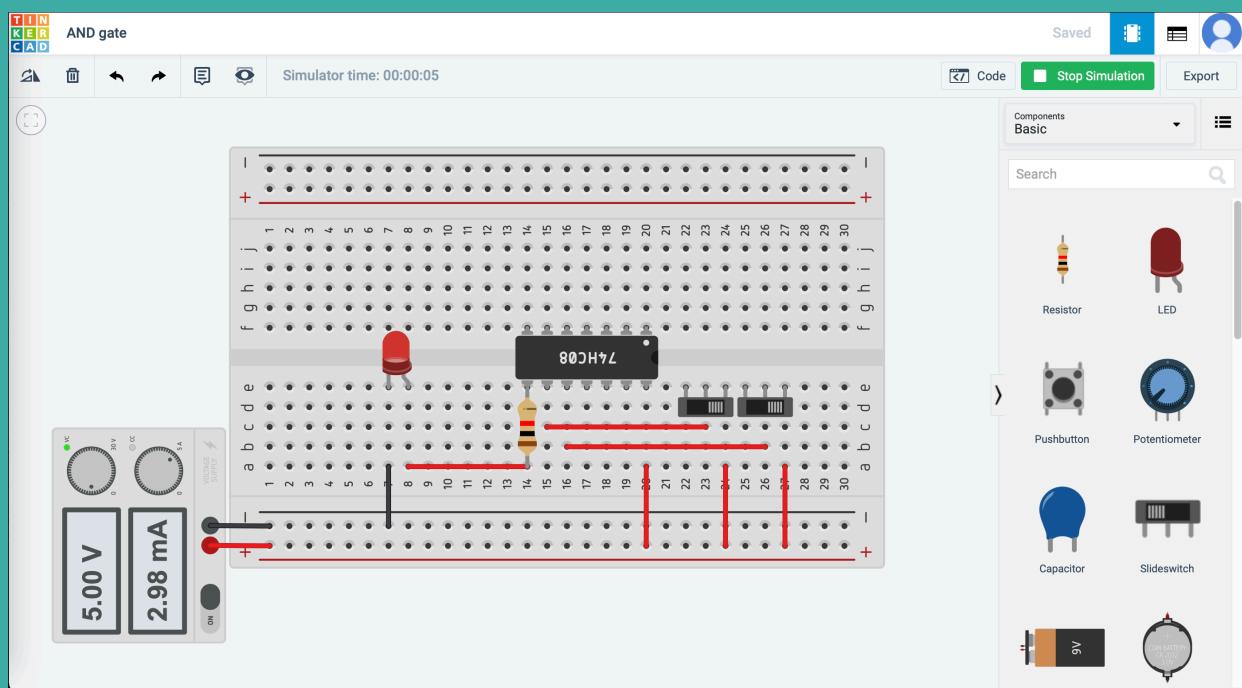

Truth Table:

X	Y	X AND Y
0	0	0
0	1	0
1	0	0
1	1	1

K maps (If Applicable):


Observations/Results: We can conclude that output of and gate in Tinkercad verifies the truth table.

Aim: Testing output of OR gate using Tinkercad

Components/ICs Used: Breadboard, Red LED, 1 kΩ Resistor, [5,5 Power Supply], Wire, slideswitch, Quad OR gate(74HC32)


Link of TINKERCAD Workspace: <https://www.tinkercad.com/things/beGVDjqiXd4>

Pin Diagram of the IC (If Applicable):

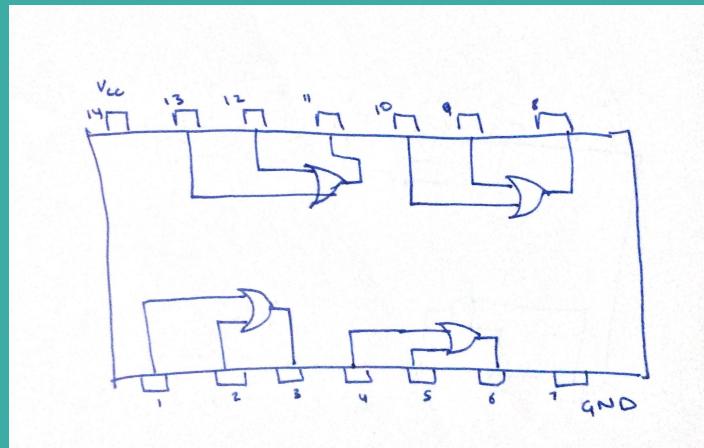

74HC32

Circuit Diagram: Screen shot

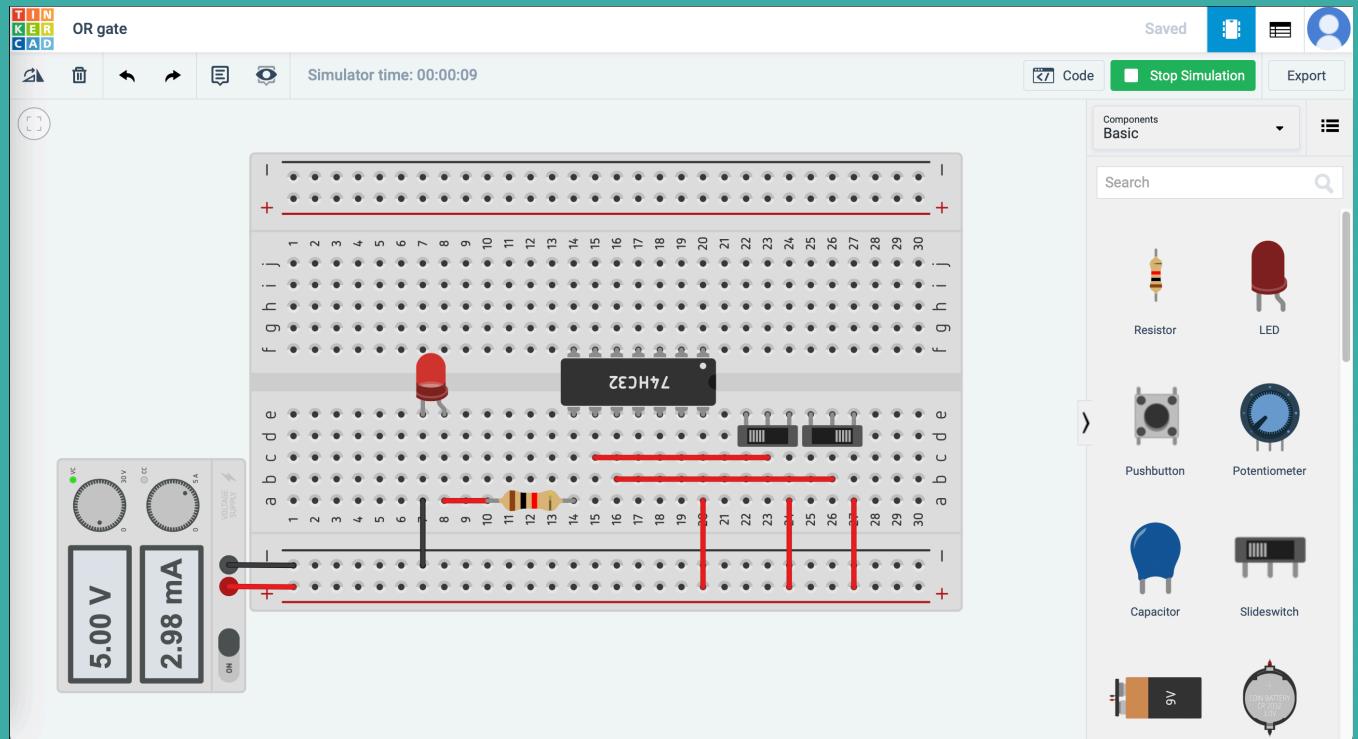

Truth Table:

X	Y	X OR Y
0	0	0
0	1	1
1	0	1
1	1	1

K maps (If Applicable):


Observations/Results: We can conclude that output of or gate in Tinkercad verifies the truth table.

Aim: Testing output of NOT gate using Tinkercad

Components/ICs Used: Breadboard, Red LED, 1 kΩ Resistor, [5,5 Power Supply], Wire, slideswitch, Hex inverter(74HC04)


Link of TINKERCAD Workspace: <https://www.tinkercad.com/things/koxfRdyyDfT>

Pin Diagram of the IC (If Applicable):

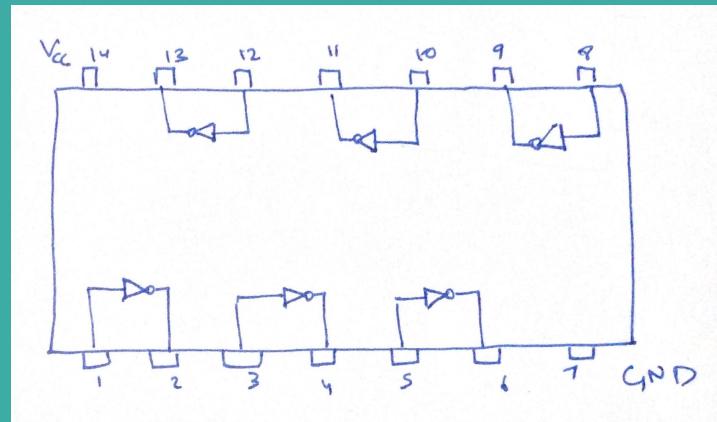

74HC04

Circuit Diagram: Screen shot

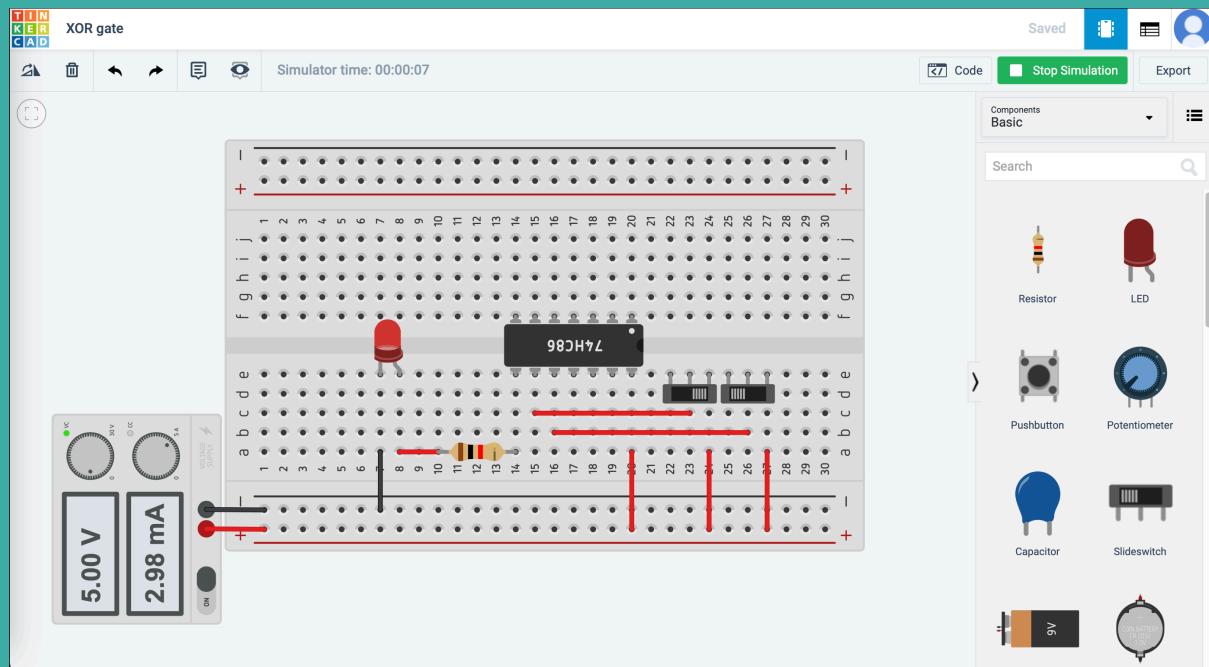

Truth Table:

<b>X</b>	<b>NOT X</b>
0	1
1	0

K maps (If Applicable):


Observations/Results: We can conclude that output of not gate in Tinkercad verifies the truth table.

Aim: Testing output of XOR gate using Tinkercad

Components/ICs Used: Breadboard, Red LED, 1 kΩ Resistor, [5,5 Power Supply], Wire, slideswitch, Quad XOR gate(74HC86)


Link of TINKERCAD Workspace: <https://www.tinkercad.com/things/20iPVVIRgwy>

Pin Diagram of the IC (If Applicable):

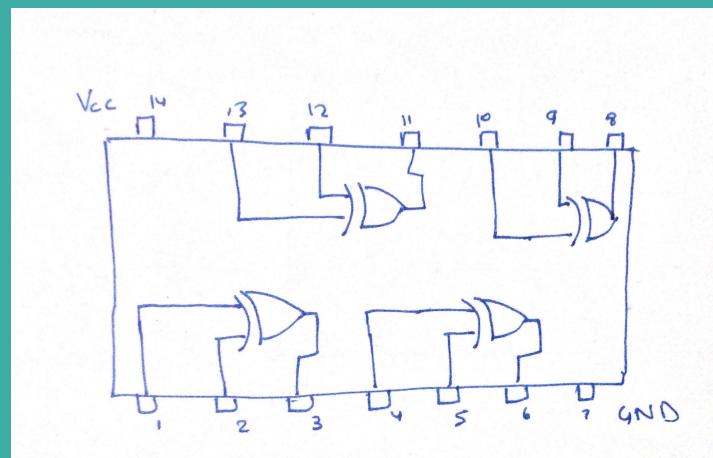

74HC86

Circuit Diagram: Screen shot

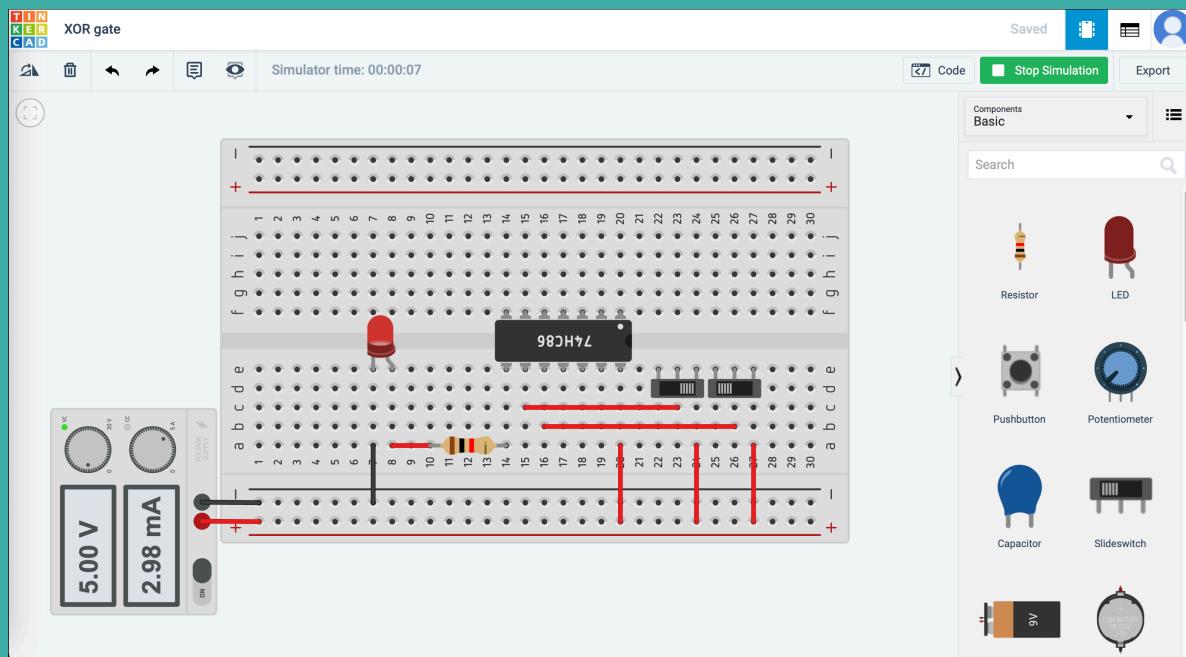

Truth Table:

<b>X</b>	<b>Y</b>	<b>X XOR Y</b>
0	0	0
0	1	1
1	0	1
1	1	0

K maps (If Applicable):


Observations/Results: We can conclude that output of xor gate in Tinkercad verifies the truth table.

Aim: Testing output of NAND gate using Tinkercad

Components/ICs Used: Breadboard, Red LED, 1 kΩ Resistor, [5.5 Power Supply], Wire, slideswitch, Quad NAND gate(74HC00)


Link of TINKERCAD Workspace: <https://www.tinkercad.com/things/6WLQNEYKkCi>

Pin Diagram of the IC (If Applicable):

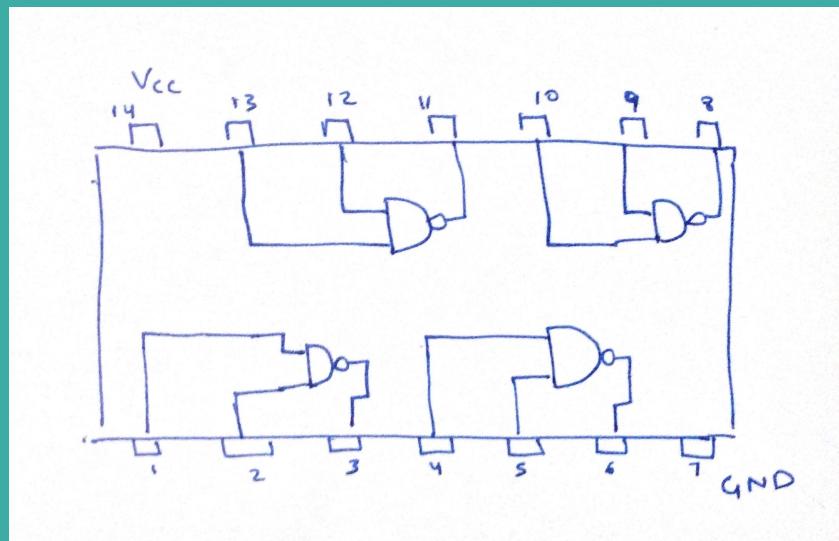

74HC00

Circuit Diagram: Screen shot

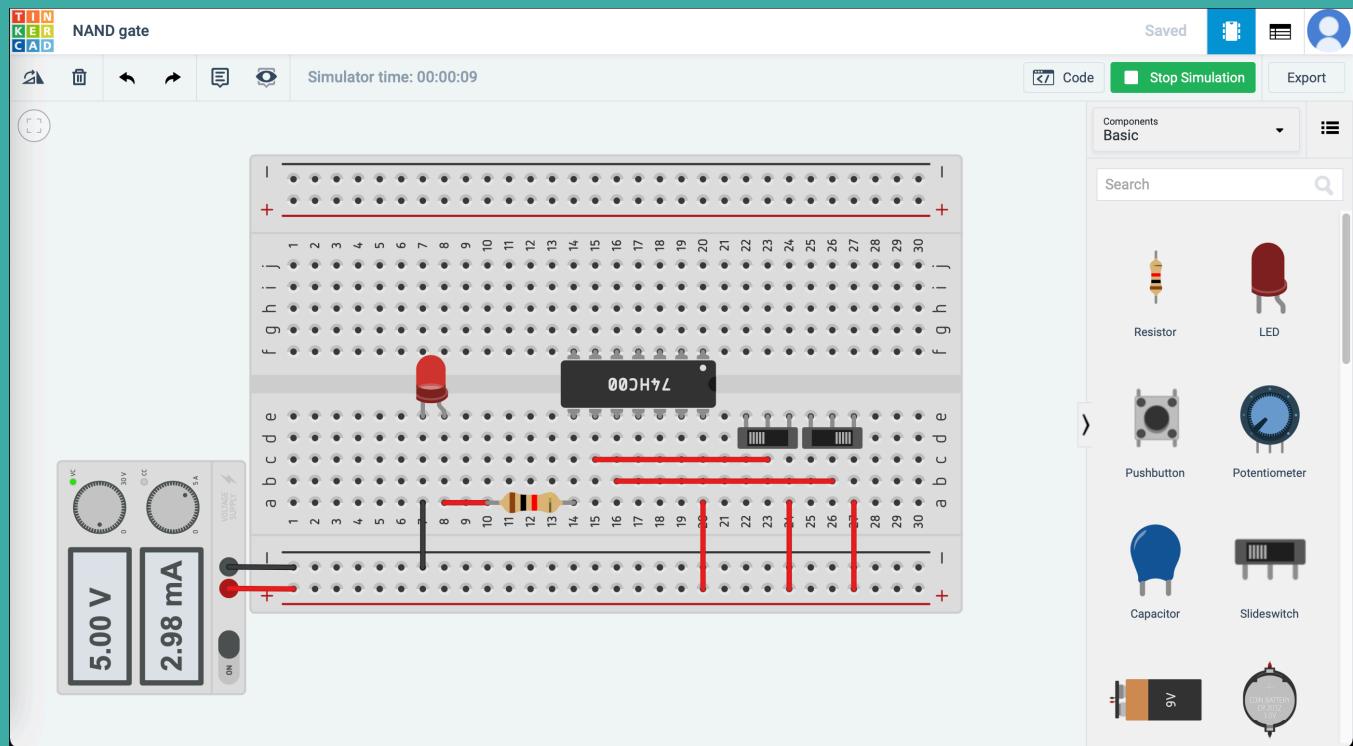

Truth Table:

<b>X</b>	<b>Y</b>	<b>X NAND Y</b>
0	0	1
0	1	1
1	0	1
1	1	0

K maps (If Applicable):


Observations/Results: We can conclude that output of nand gate in Tinkercad verifies the truth table.

Aim: Testing output of NOR gate using Tinkercad

Components/ICs Used: Breadboard, Red LED, 1 kΩ Resistor, [5,5 Power Supply], Wire, slideswitch, Quad NOR gate(74HC02)


Link of TINKERCAD Workspace: <https://www.tinkercad.com/things/2mrKGG5DGuT>

Pin Diagram of the IC (If Applicable):

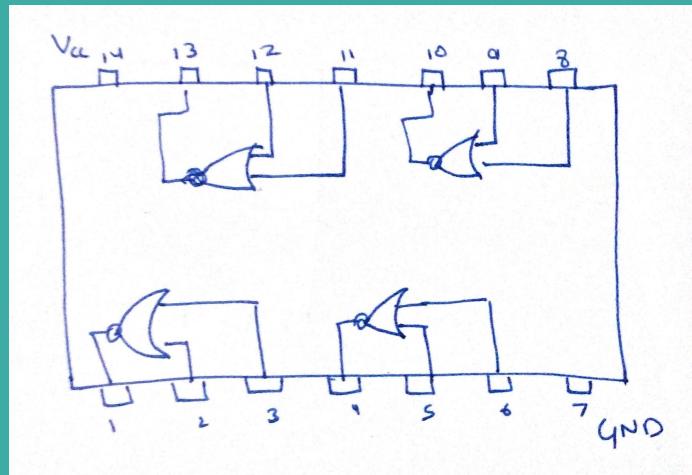

74HC02

Circuit Diagram: Screen shot

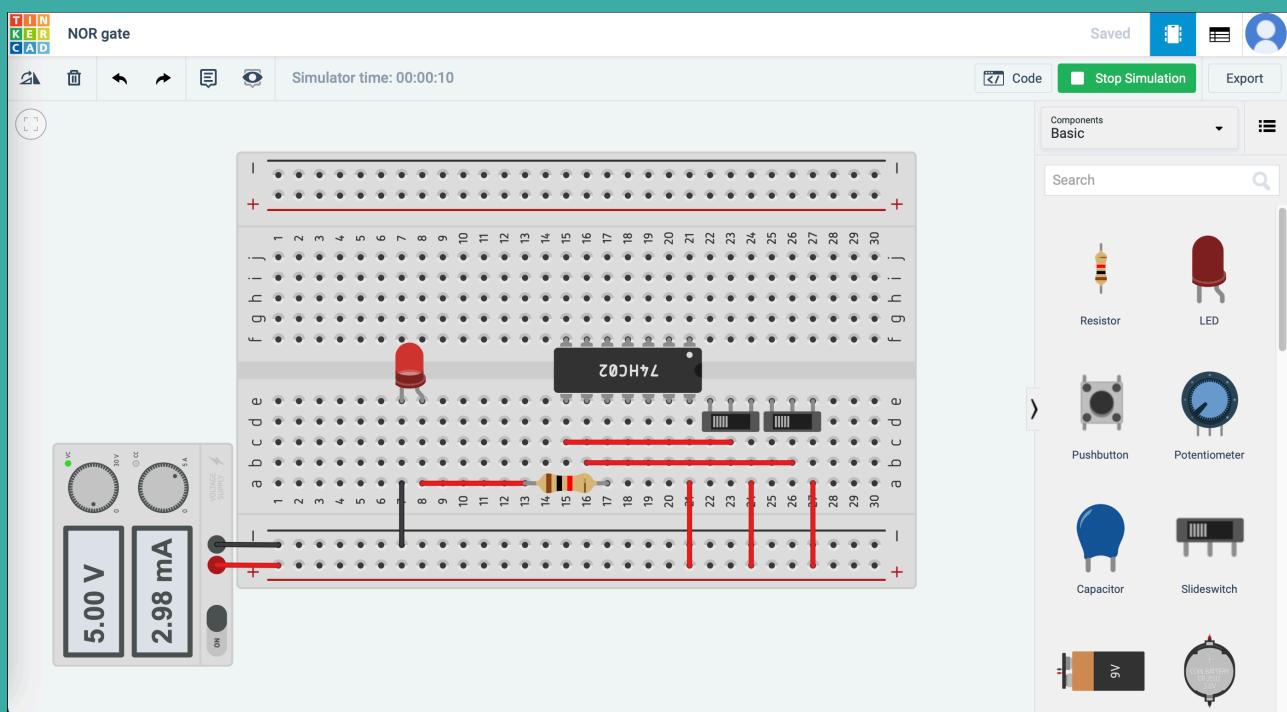

Truth Table:

<b>X</b>	<b>Y</b>	<b>X NOR Y</b>
0	0	1
0	1	0
1	0	0
1	1	0

K maps (If Applicable):

Observations/Results: We can conclude that output of nor gate in Tinkercad verifies the truth table.