



INDRAPRASTHA INSTITUTE *of*  
INFORMATION TECHNOLOGY  
DELHI

Department  
of  
Electronics & Communication Engineering

ECE111|Digital Circuits

**Dr. G.S. Visweswaran**

Lab\_6:  
Combinational Circuit Design

Student Name : Aayush Gakhar  
Roll No. : 2020006  
Date : 14/3/2021

# Part A. Decoder Circuit for generating BCD Code from Encrypted code


Aim: Designing and testing of a circuit for decryption/decoding of an incoming digital signal which is encrypted by some set of rules which are:

An encrypted communication system sends decimal digits encoded by a 4-bit binary code  $C_3 C_2 C_1 C_0$  according to the following scheme, where  $N$  denotes the value of the digit:

For  $4 \geq N \geq 0$ ,  $C_3 C_2 C_1 C_0 = 13 - N$  (in decimal), and  
for  $9 \geq N \geq 5$ ,  $C_3 C_2 C_1 C_0 = N - 3$  (in decimal).


Components/ICs Used: Input, ConstantVal, Nand gate, Wire, splitter(Bitwidth=4), Hexdisplay

Circuit Diagram:

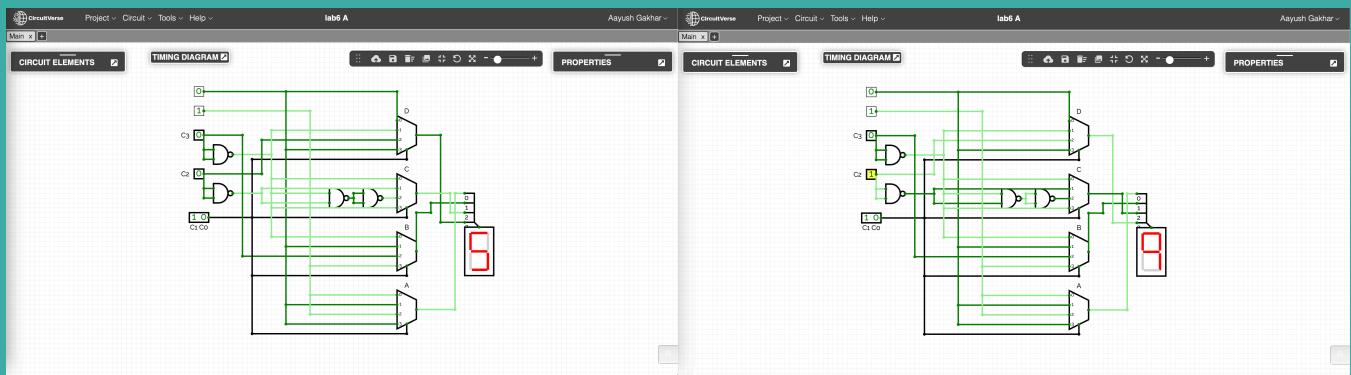

Input = 2(0010) Output = 5

Input = 6(0110) Output = 9

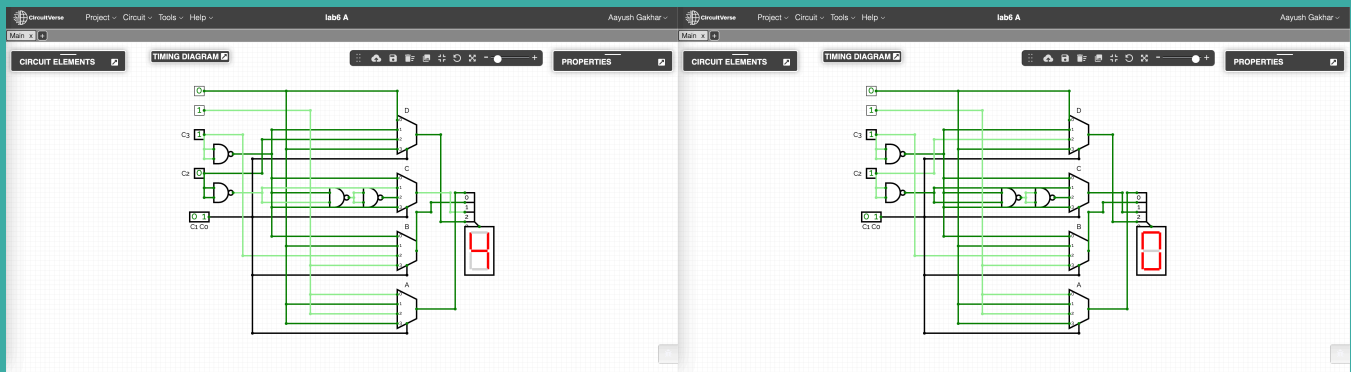

Input = 9(1001) Output = 4

Input = 13(1101) Output = 0

Truth Table:

Encr. Code	C3	C2	C1	C0	DE of N	D	C	B	A
0	0	0	0	0	X	X	X	X	X
1	0	0	0	1	X	X	X	X	X
2	0	0	1	0	5	0	1	0	1
3	0	0	1	1	6	0	1	1	0
4	0	1	0	0	7	0	1	1	1
5	0	1	0	1	8	1	0	0	0
6	0	1	1	0	9	1	0	0	1
7	0	1	1	1	X	X	X	X	X
8	1	0	0	0	X	X	X	X	X
9	1	0	0	1	4	0	1	0	0
10	1	0	1	0	3	0	0	1	1
11	1	0	1	1	2	0	0	1	0
12	1	1	0	0	1	0	0	0	1
13	1	1	0	1	0	0	0	0	0
14	1	1	1	0	X	X	X	X	X
15	1	1	1	1	X	X	X	X	X

K maps (If Applicable):

D		C1 C0			
		0 0	0 1	1 1	1 0
C3 C2	0 0	X	X	0	0
	0 1	0	1	X	1
	1 1	0	0	X	X
	1 0	X	0	0	0

C1 C0	0 0	0 1	1 1	1 0
I/O OF MUX FOR D	0	C3'	0	C2

C		C1 C0			
		0 0	0 1	1 1	1 0
C3 C2	0 0	X	X	1	1
	0 1	1	0	X	0
	1 1	0	0	X	X
	1 0	X	1	0	0

C1 C0	0 0	0 1	1 1	1 0
I/O OF MUX FOR C	C3'	C2'	C3'	C3' C2'

B		C1 C0			
		0 0	0 1	1 1	1 0
C3 C2	0 0	X	X	1	0
	0 1	1	0	X	0
	1 1	0	0	X	X
	1 0	X	0	1	1

C1 C0	0 0	0 1	1 1	1 0
I/O OF MUX FOR B	C3'	0	1	C3

A		C1 C0			
		0 0	0 1	1 1	1 0
C3 C2	0 0	X	X	0	1
	0 1	1	0	X	1
	1 1	1	0	X	X
	1 0	X	0	0	1

C1 C0	0 0	0 1	1 1	1 0
I/O OF MUX FOR A	1	0	0	1

FINAL				
C1 C0	0 0	0 1	1 0	1 1
D	0	C3'	C2	0
C	C3'	C2'	C3' C2'	C3'
B	C3'	0	C3	1
A	1	0	1	0

Observations/Results: The hex display works according to the truth table


Applications: Decoders are greatly used in applications where the particular output or group of outputs to be activated only on the occurrence of a specific combination of input levels. Specific output is provided for specific input.

## Part B. Divider Circuit for 2-bit Binary Numbers

Aim: Designing and testing a circuit for dividing a 2-bit number  $N_1 N_0$  by another 2-bit number  $D_1 D_0$  ( $D_1 D_0 \neq 0$ ) to generate a 2-bit quotient  $Q_1 Q_0$  and a 2-bit remainder  $R_1 R_0$ .


Components/ICs Used: Input, ConstantVal, Nand gate, Wire, splitter(Bitwidth=4), Hexdisplay

Circuit Diagram:

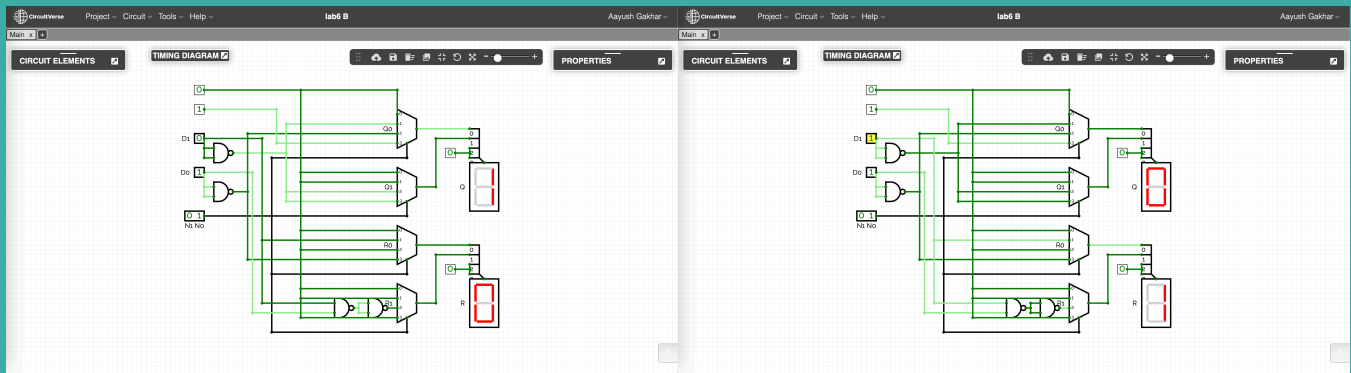

Input( $N_1 N_0 D_1 D_0$ ) = 0101  
Output( $Q R$ ) = 1 0

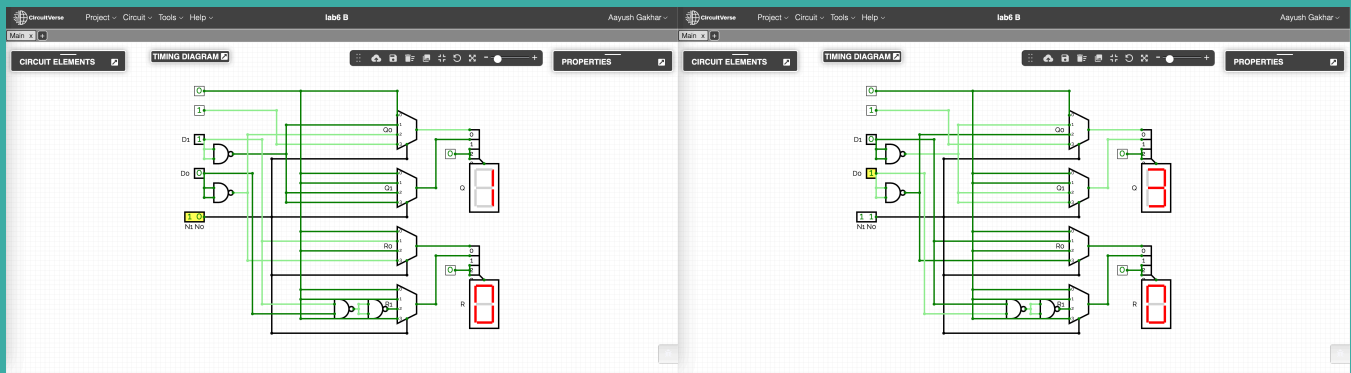Input( $N_1 N_0 D_1 D_0$ ) = 0111  
Output( $Q R$ ) = 0 1



Input( $N_1 N_0 D_1 D_0$ ) = 1010  
Output( $Q R$ ) = 1 0

Input( $N_1 N_0 D_1 D_0$ ) = 1101  
Output( $Q R$ ) = 3 0

Truth Table:

N1	N0	D1	D0	Q1	Q0	R1	R0
0	0	0	0	X	X	X	X
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	X	X	X	X
0	1	0	1	0	1	0	0
0	1	1	0	0	0	0	1
0	1	1	1	0	0	0	1
1	0	0	0	X	X	X	X
1	0	0	1	1	0	0	0
1	0	1	0	0	1	0	0
1	0	1	1	0	0	1	0
1	1	0	0	X	X	X	X
1	1	0	1	1	1	0	0
1	1	1	0	0	1	0	1
1	1	1	1	0	1	0	0



K maps (If Applicable):

Q1		N1 N0			
		0 0	0 1	1 1	1 0
D1 D0	0 0	X	X	X	X
	0 1	0	0	1	1
	1 1	0	0	0	0
	1 0	0	0	0	0

N1 N0	0 0	0 1	1 1	1 0
I/O OF MUX FOR Q1	0	0	D1'	D1'

Q0		N1 N0			
		0 0	0 1	1 1	1 0
D1 D0	0 0	X	X	X	X
	0 1	0	1	1	0
	1 1	0	0	1	0
	1 0	0	0	1	1

N1 N0	0 0	0 1	1 1	1 0
I/O OF MUX FOR Q0	0	D1'	1	D0'

R1		N1 N0			
		0 0	0 1	1 1	1 0
D1 D0	0 0	X	X	X	X
	0 1	0	0	0	0
	1 1	0	0	0	1
	1 0	0	0	0	0

N1 N0	0 0	0 1	1 1	1 0
I/O OF MUX FOR R1	0	0	0	D1 D0

R0		N1 N0			
		0 0	0 1	1 1	1 0
D1 D0	0 0	X	X	X	X
	0 1	0	0	0	0
	1 1	0	1	0	0
	1 0	0	1	1	0

N1 N0	0 0	0 1	1 1	1 0
I/O OF MUX FOR R0	0	D1	D0'	0

FINAL				
N1 N0	0 0	0 1	1 0	1 1
Q1	0	0	D1'	D1'
Q0	0	D1'	D0'	1
R1	0	0	D1 D0	0
R0	0	D1	0	D0'

Observations/Results: The hex display works according to the truth table.

Applications: Dividers are used in ALU of chips to do basic division operations. This is a combinational circuit and combinational circuits have a wide variety of uses such as calculators, digital measuring techniques, computers, digital processing, automatic control of machines, industrial processing, digital communications, etc.