



INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY
DELHI

Department
of
Electronics & Communication Engineering

ECE111|Digital Circuits

Dr. G.S. Visweswaran

END_SEM_Project:
Synchronous decade UP counter


Student Name : Aayush Gakhar
Roll No. : 2020006
Date : 06/04/2021

Aim: Implement a Synchronous decade UP counter in Circuit-verse and verify its operation. Realize inputs of D-flip flops with 4-input multiplexers, using Q1Q0 as the select inputs. Realize the Data inputs of the multiplexers with NOR gates.


Components/ICs Used: 4:1 Mux, wire, clock, D flip flop, splitter, hex display

Youtube link: https://youtu.be/QPF-Imqr_NY

Screenshot:

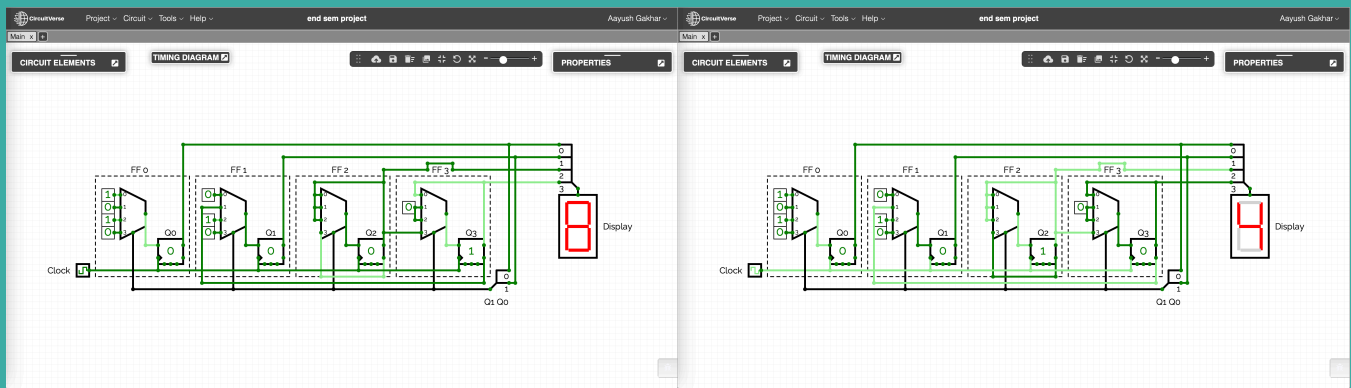

Block Diagram/Circuit Diagram:

 

Truth Table:

Decimal	Q ₃	Q ₂	Q ₁	Q ₀
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

State Transition Table :

PS	NS	D ₃	D ₂	D ₁	D ₀
0 0 0 0	0 0 0 1	0	0	0	1
0 0 0 1	0 0 1 0	0	0	1	0
0 0 1 0	0 0 1 1	0	0	1	1
0 0 1 1	0 1 0 0	0	1	0	0
0 1 0 0	0 1 0 1	0	1	0	1
0 1 0 1	0 1 1 0	0	1	1	0
0 1 1 0	0 1 1 1	0	1	1	1
0 1 1 1	1 0 0 0	1	0	0	0
1 0 0 0	1 0 0 1	1	0	0	1
1 0 0 1	0 0 0 0	0	0	0	0

K maps (If Applicable):

D₀		Q₁ Q₀			
		0 0	0 1	1 1	1 0
Q₃ Q₂	0 0	1	0	0	1
	0 1	1	0	0	1
	1 1	X	X	X	X
	1 0	1	0	X	X

Q₁ Q₀	0 0	0 1	1 1	1 0
I/p OF MUX FOR D₀	1	0	0	1

D₁		Q₁ Q₀			
		0 0	0 1	1 1	1 0
Q₃ Q₂	0 0	0	1	0	1
	0 1	0	1	0	1
	1 1	X	X	X	X
	1 0	0	0	X	X

Q₁ Q₀	0 0	0 1	1 1	1 0
I/p OF MUX FOR D₁	0	Q ₃ '	0	1

D_2		$Q_1 Q_0$			
		0 0	0 1	1 1	1 0
$Q_3 Q_2$	0 0	0	0	1	0
	0 1	1	1	0	1
	1 1	X	X	X	X
	1 0	0	0	X	X

$Q_1 Q_0$	0 0	0 1	1 1	1 0
I/p OF MUX FOR D_2	Q_2	Q_2	Q_2'	Q_2

D_3		$Q_1 Q_0$			
		0 0	0 1	1 1	1 0
$Q_3 Q_2$	0 0	0	0	0	0
	0 1	0	0	1	0
	1 1	X	X	X	X
	1 0	1	0	X	X

$Q_1 Q_0$	0 0	0 1	1 1	1 0
I/p OF MUX FOR D_3	Q_3	0	Q_2	0

Logical expressions:

$$D_0 = Q_0'$$

$$D_1 = Q_1'Q_0Q_3' + Q_1Q_0'$$

$$D_2 = Q_0'Q_2 + Q_0'Q_2' + Q_1Q_0Q_2'$$

$$D_3 = Q_2Q_1Q_0 + Q_3Q_0'$$

Observations/Results: The display shows from 0 to 9 as given in truth table.

Applications of the experiment:

Clock generation

Clock division

In frequency counting circuits