



INDRAPRASTHA INSTITUTE *of*  
INFORMATION TECHNOLOGY  
DELHI

Department  
of  
Electronics & Communication Engineering

ECE111|Digital Circuits

**Dr. G.S. Visweswaran**

Lab\_9:  
Ripple Counters

Student Name : Aayush Gakhar  
Roll No. : 2020006  
Date : 4/4/2021

## Part A. Binary Ripple Counter

Aim: Implement a Binary Ripple Counter in Tinkercad and verify its operation.

Components/ICs Used: Breadboard, Red LED, 1 kΩ Resistor, [5,5 Power Supply], Wire, slideswitch, dual JK flip-flop IC (74HC73), Function generator


Link of TINKERCAD Workspace:

UP counter: <https://www.tinkercad.com/things/7VRsQYJacOD>


DOWN counter: <https://www.tinkercad.com/things/iBxBdBZm7A1>

Circuit screenshot:


Up counter:

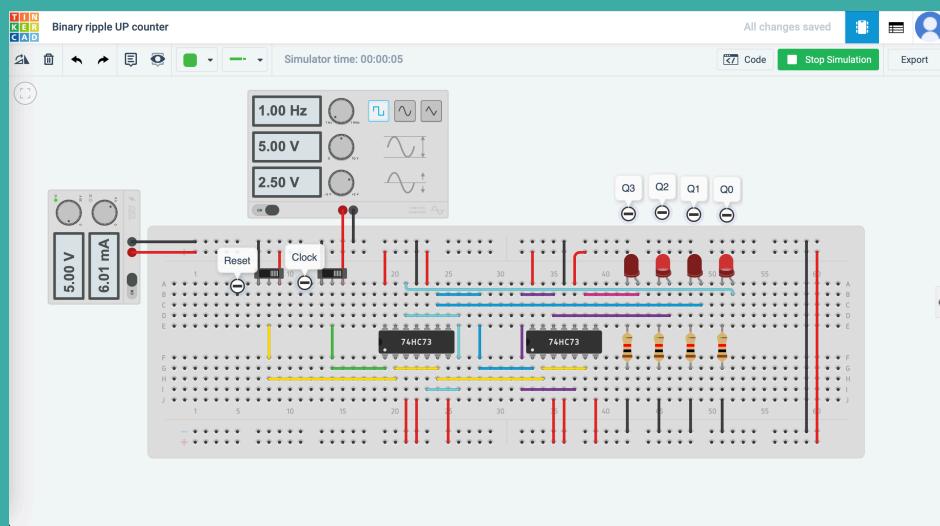


Down counter:

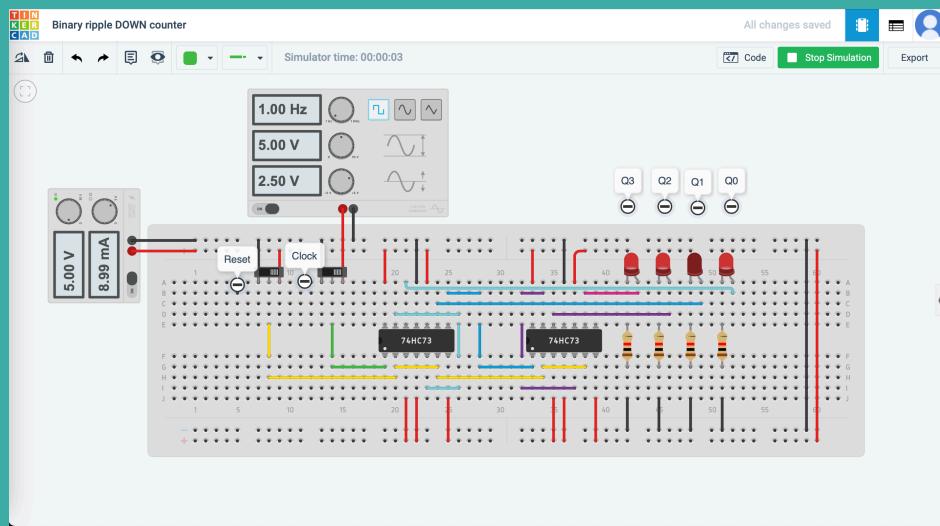

Circuit diagram:  
UP counter:

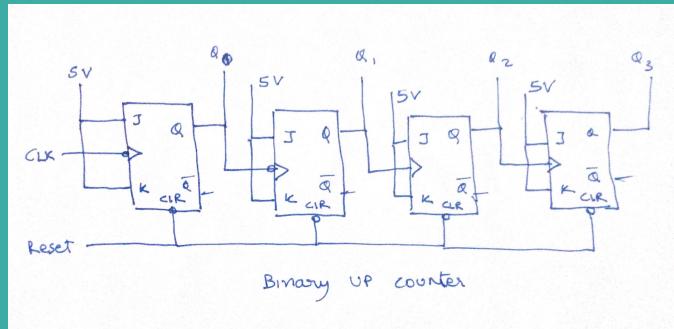

DOWN counter:

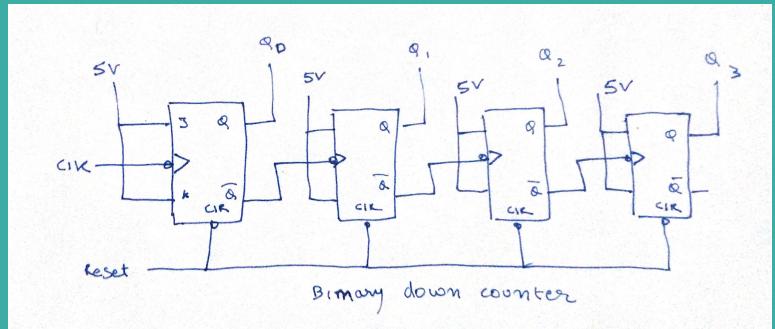

Decimal to binary Truth Table:

Decim al	$Q_3$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1

State Table:

For Up Counter:

		<b>Present State</b>	<b>Next State</b>
<b>Reset</b>	<b>Clock</b>	$Q_3\ Q_2\ Q_1\ Q_0$	$Q_3\ Q_2\ Q_1\ Q_0$
0	X	XXXX	0000
1	0	$Q_n$	$Q_n$
1	1	0000	0001
1	1	0001	0010
1	1	0010	0011
1	1	0011	0100
1	1	0100	0101
1	1	0101	0110
1	1	0110	0111
1	1	0111	1000
1	1	1000	1001
1	1	1001	1010
1	1	1010	1011
1	1	1011	1100
1	1	1100	1101
1	1	1101	1110
1	1	1110	1111
1	1	1111	0000

For Down Counter:

		<b>Present State</b>	<b>Next State</b>
<b>Reset</b>	<b>Clock</b>	$Q_3 Q_2 Q_1 Q_0$	$Q_3 Q_2 Q_1 Q_0$
0	X	XXXX	1111
1	0	$Q_n$	$Q_n$
1	1	1111	1110
1	1	1110	1101
1	1	1101	1100
1	1	1100	1011
1	1	1011	1010
1	1	1010	1001
1	1	1001	1000
1	1	1000	0111
1	1	0111	0110
1	1	0110	0101
1	1	0101	0100
1	1	0100	0011
1	1	0011	0010
1	1	0010	0001
1	1	0001	0000
1	1	0000	1111

Observations/Results: The output matches with the truth table and the LEDs glow showing 0 to 15 in binary.

Justifications: The up and down counter work by taking the output of a flipflop as input to another flipflop. This works as a frequency divider and the frequency is halved each flipflop. The 4 outputs appear to count in binary.

Applications of the experiment: counters have following applications:

- Frequency counters
- Digital clocks
- Analog to digital convertors.
- With some changes in their design, counters can be used as frequency divider circuits. The frequency divider circuit is that which divides the input frequency exactly by '2'.
- In time measurement. That means calculating time in timers such as electronic devices like ovens and washing machines.


## Part B. Decade Ripple Counter

Aim: Implement a Decade Ripple Counter in Tinkercad and verify its operation.


Components/ICs Used: Breadboard, Red LED, 1 kΩ Resistor, [5.5 Power Supply], Wire, slideswitch, dual JK flip-flop IC(74HC73), NAND IC(74HC00), seven segment decoder(CD4511), Function generator

Link of TINKERCAD Workspace: <https://www.tinkercad.com/things/0MnEOXiPRq6>

Circuit screenshot:

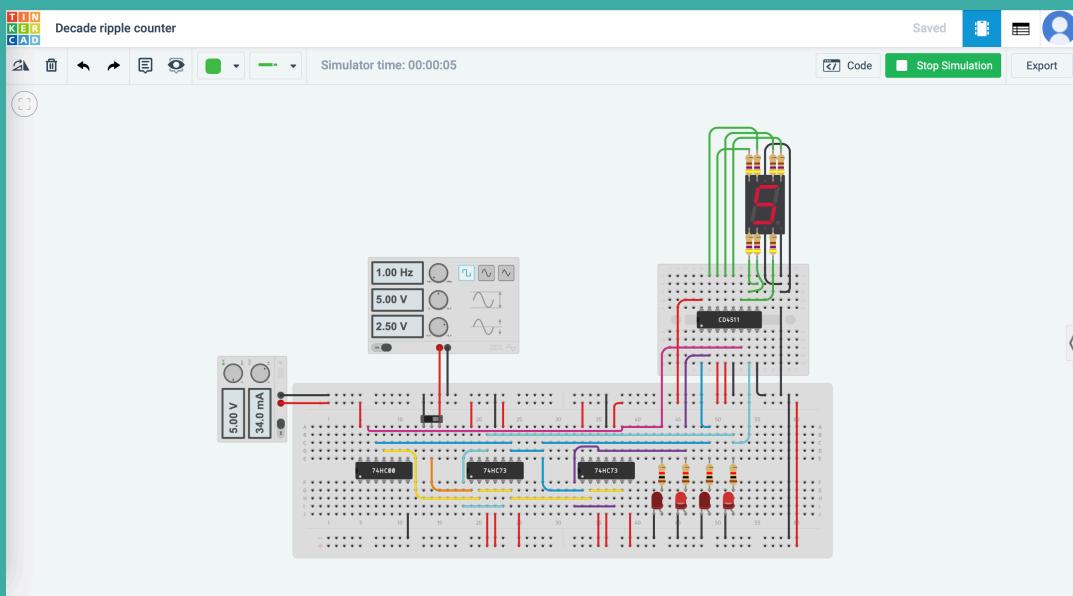

Circuit diagram:

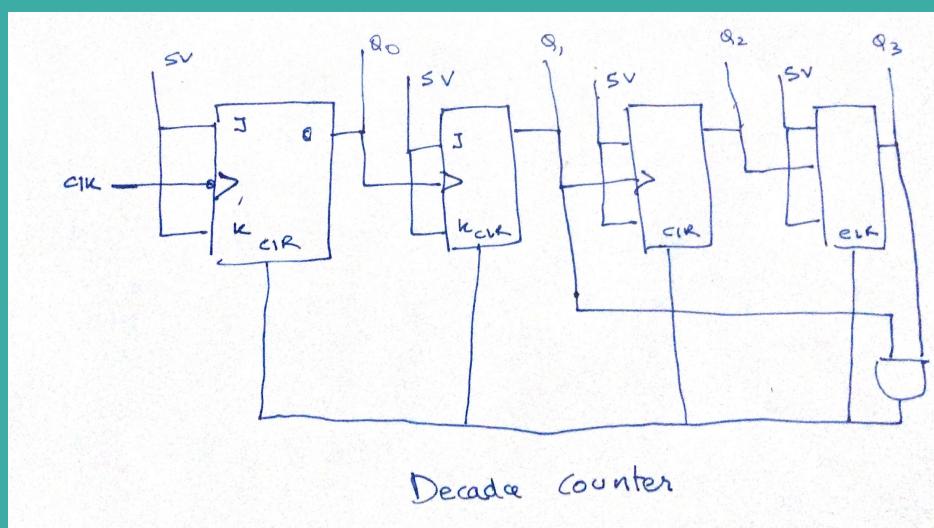

Decimal to binary Truth Table:

Decim al	$Q_3$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

State Table:

	Present State	Next State
Clock	$Q_3 Q_2 Q_1 Q_0$	$Q_3 Q_2 Q_1 Q_0$
0	$Q_n$	$Q_n$
1	0 0 0 0	0 0 0 1
1	0 0 0 1	0 0 1 0
1	0 0 1 0	0 0 1 1
1	0 0 1 1	0 1 0 0
1	0 1 0 0	0 1 0 1
1	0 1 0 1	0 1 1 0
1	0 1 1 0	0 1 1 1
1	0 1 1 1	1 0 0 0
1	1 0 0 0	1 0 0 1
1	1 0 0 1	0 0 0 0

**Observations/Results:** The output matches with the truth table and the 7 segment display shows from 0 to 9.

**Justifications:** This is an up counter with the reset connected to Q3 AND Q1. So when the Q3 and Q1 are both 1 (at decimal 10) the up counter resets to 0 0 0 0.

**Applications of the experiment:** counters have following applications:

- Decade counters are used in clock circuits, frequency dividers, state machines, and sequencers.
- Clock division.
- Integrated oscillator.
- In frequency counting circuits